## Appendix for: Large-Signal Stability of Power Systems with Mixtures of GFL, GFM and GSP Inverters

Yifan Zhang, Student Member, IEEE, Yunjie Gu, Senior Member, IEEE, Sijia Geng, Senior Member, IEEE, Yue Zhu, Members, IEEE, Hsiao-Dong Chiang, Fellows, IEEE, Timothy C. Green, Fellows, IEEE

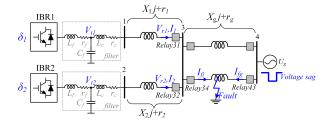


Fig. 2. Two-inverter system and detailed configurations used in EMT simulation.

## APPENDIX B EMT SIMULATION PARAMETERS

 $\begin{tabular}{ll} TABLE~B1\\ SYSTEM~PARAMETERS~IN~TWO~PARALLELED~GFL~INVERTERS~SYSTEM \end{tabular}$ 

Parameters	Value (p.u.)
Base frequency $\omega_s$	50 Hz
Grid voltage $U_g$	1
DC voltage $U_{dc}$	2.5
LCL Filter impedance $L_f j + r_f$	0.2j + 0.002
LCL Filter capacitance $C_f$	0.01
Inner current control loop bandwidth	1 kHz
PLL controller of IBR1 $k_{pll1}$	$10 \times 2\pi$
PLL controller of IBR1 $k_i$	$2\pi$
PLL controller of IBR2 $k_{pll2}$	$10 \times 2\pi$
PLL controller of IBR2 $k_i$	$2\pi$
Frequency limit of PLL $\omega_{limit}$	$\pm 0.2$
Current reference of IBR1 $I_{1d}$	0.8
Current reference of IBR2 $I_{2d}$	0.4
Line impedance $Z_1$	0.2j+0.002
Line impedance $Z_2$	0.2j+0.002
Line impedance $Z_g$	0.35j or 0.4j
Fault resistance $R_f$	0.02

 $\label{eq:table B2} \textbf{System Parameters in GFL - GFM(GSP) Inverters System}$ 

$\begin{array}{ c c c c } \hline \text{Parameters} & \text{Value (p.u.)} \\ \hline \text{Base frequency } \omega_s & 50 \text{ Hz} \\ \hline \text{Grid voltage } U_g & 1 \\ \hline \text{Impedance } Z_1 & 0.5 \text{j+0.025} \\ \hline \text{Impedance (include virtual one) } Z_2 & 0.1 \text{j+0.002} \\ \hline \text{Impedance } 2Z_g & 0.6 \text{j+0.03} \\ \hline \text{Fault resistance } R_f & 0.001 \\ \hline \text{Fault position (from the infinite bus)} & 0.8 \\ \hline \hline \text{IBR1 - GFL} \\ \hline \hline \text{Inner current control loop bandwidth} & 1 \text{ kHz} \\ \hline \hline \end{array}$
Grid voltage $U_g$ 1 Impedance $Z_1$ 0.5j+0.025 Impedance (include virtual one) $Z_2$ 0.1j+0.002 Impedance $2Z_g$ 0.6j+0.03 Fault resistance $R_f$ 0.001 Fault position (from the infinite bus) 0.8 IBR1 - GFL
$\begin{array}{c cccc} \text{Impedance } Z_1 & 0.5 \text{j}+0.025 \\ \text{Impedance (include virtual one)} & Z_2 & 0.1 \text{j}+0.002 \\ \text{Impedance } 2Z_g & 0.6 \text{j}+0.03 \\ \text{Fault resistance } R_f & 0.001 \\ \text{Fault position (from the infinite bus)} & 0.8 \\ \hline \text{IBR1 - GFL} & \end{array}$
$ \begin{array}{c cccc} \text{Impedance (include virtual one)} & Z_2 & 0.1 \text{j+0.002} \\ \text{Impedance} & 2Z_g & 0.6 \text{j+0.03} \\ \text{Fault resistance} & R_f & 0.001 \\ \text{Fault position (from the infinite bus)} & 0.8 \\ \hline \text{IBR1 - GFL} \\ \end{array} $
Fault resistance $R_f$ 0.001  Fault position (from the infinite bus) 0.8  IBR1 - GFL
Fault position (from the infinite bus) 0.8  IBR1 - GFL
IBR1 - GFL
Inner current control loop bandwidth 1 kHz
vonitor roop cuito ricon
PLL controller $k_{pll1}$ $2.5 \times 2\pi$
PLL controller $k_i$ $0.25 \times 2\pi$
Frequency limit of PLL $\omega_{limit}$ $\pm 0.2$
Current reference $I_{1d}$ 1
DC voltage $U_{dc}$ 2.5
LCL filter impedance $L_f j + r_f$ 0.2j+0.02
LCL filter capacitance $C_f$ 0.01
IBR2 - GFM
$P - \omega$ droop gain $k_{p-\omega}$ $2.5 \times 2\pi$
Power reference $P_{ref}$ 0.6 in Section IV-A,
0 in Section IV-B
Voltage reference $V_{gfm}$ 1
Inner voltage control loop bandwidth 200 Hz
Inner current control loop bandwidth 1 kHz
LCL filter impedance $L_f j + r_f$ 0.2j+0.02
LCL filter capacitance $C_f$ 0.1
Current limit $I_{limit}$ 2
$P-\omega$ droop time constant $\tau_p$
IBR2 - GSP
Voltage droop $m_q$ 1 or 4 in Section IV-A
Voltage reference $V_{ref}$ 2 in Section IV-B
Current reference $I_{2d}$ 0.6 in Section IV-A,
$\begin{array}{c} \text{Current reference } T_{2d} \\ \text{O in Section IV-A}, \\ \end{array}$
Voltage droop filter time scale $\tau_v$
PLL controller $k_{pll2}$ $k_{p-\omega} \cdot \frac{1}{X_{2sum}}$

TABLE B3
System Parameters in the GFM - GSP Inverters System

Impedance $Z_1$	0.5j+0.025
Impedance $Z_2$	0.1j+0.002
Impedance $2Z_g$	0.6j+0.03
Fault resistance $R_f$	0.001
Fault position (from the infinite bus)	0.8
IBR1 - GFM	
$P - \omega$ droop gain $k_{p-\omega}$	$2.5 \times 2\pi$
Power reference $P_{ref}$	0.8
Voltage reference $V_{gfm}$	1
Inner voltage control loop bandwidth	200 Hz
Inner current control loop bandwidth	1 kHz
Current limit $I_{limit}$	2
$P-\omega$ droop time constant $ au_p$	$1/(25 \times 2\pi)$
IBR2 - GSP	
Voltage droop $m_q$	0, 2, or 4
Voltage reference $V_{ref}$	1
Current reference $I_{2d}$	0.2
Voltage droop filter time scale $ au_v$	$1/(50 \times 2\pi)$
PLL controller $k_{pll2}$	$6 \times 2\pi$
PLL controller $k_i$	$0.6 \times 2\pi$